

 

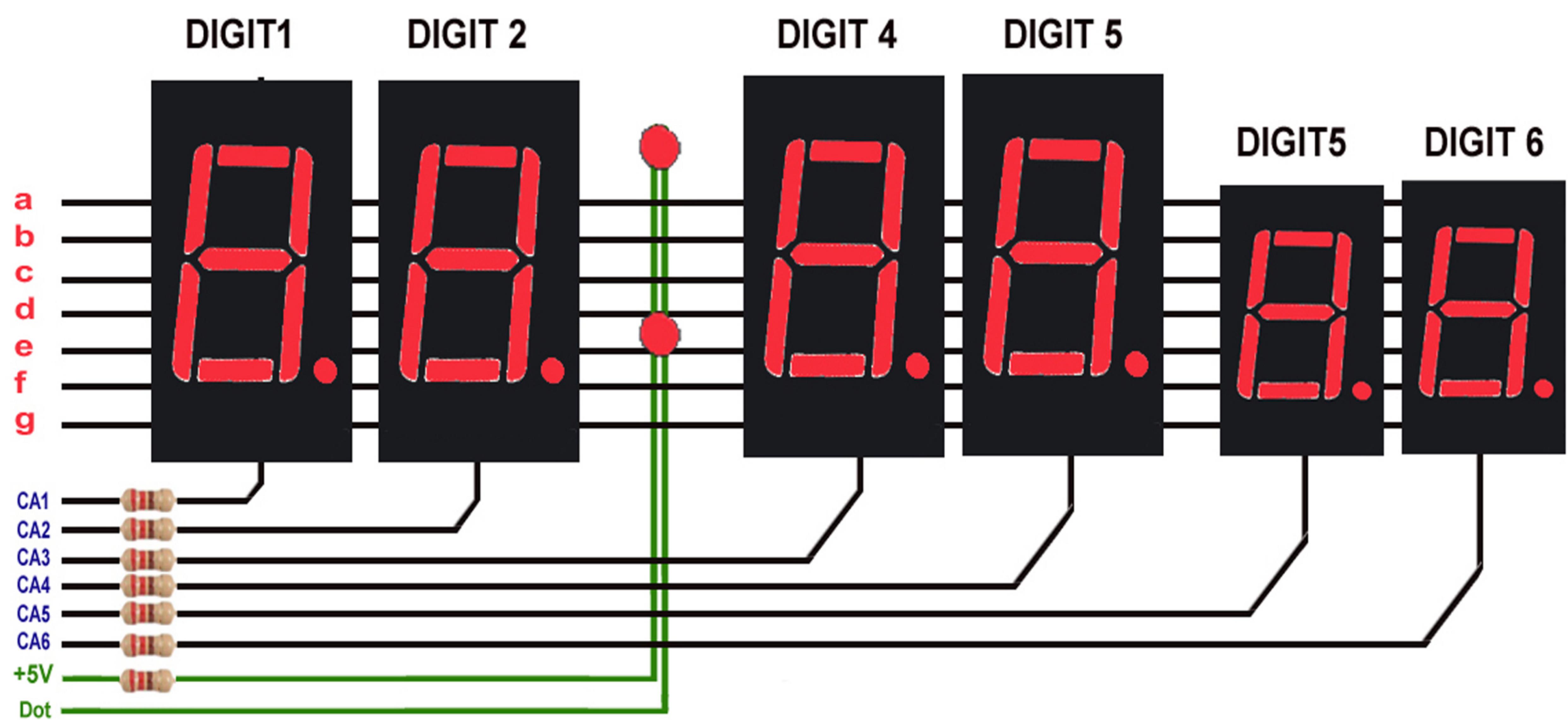
# LED SEVEN SEGMENT CLOCK WITH SECOND , HOUR CHIME AND ALARM USING ARUDINO NANO



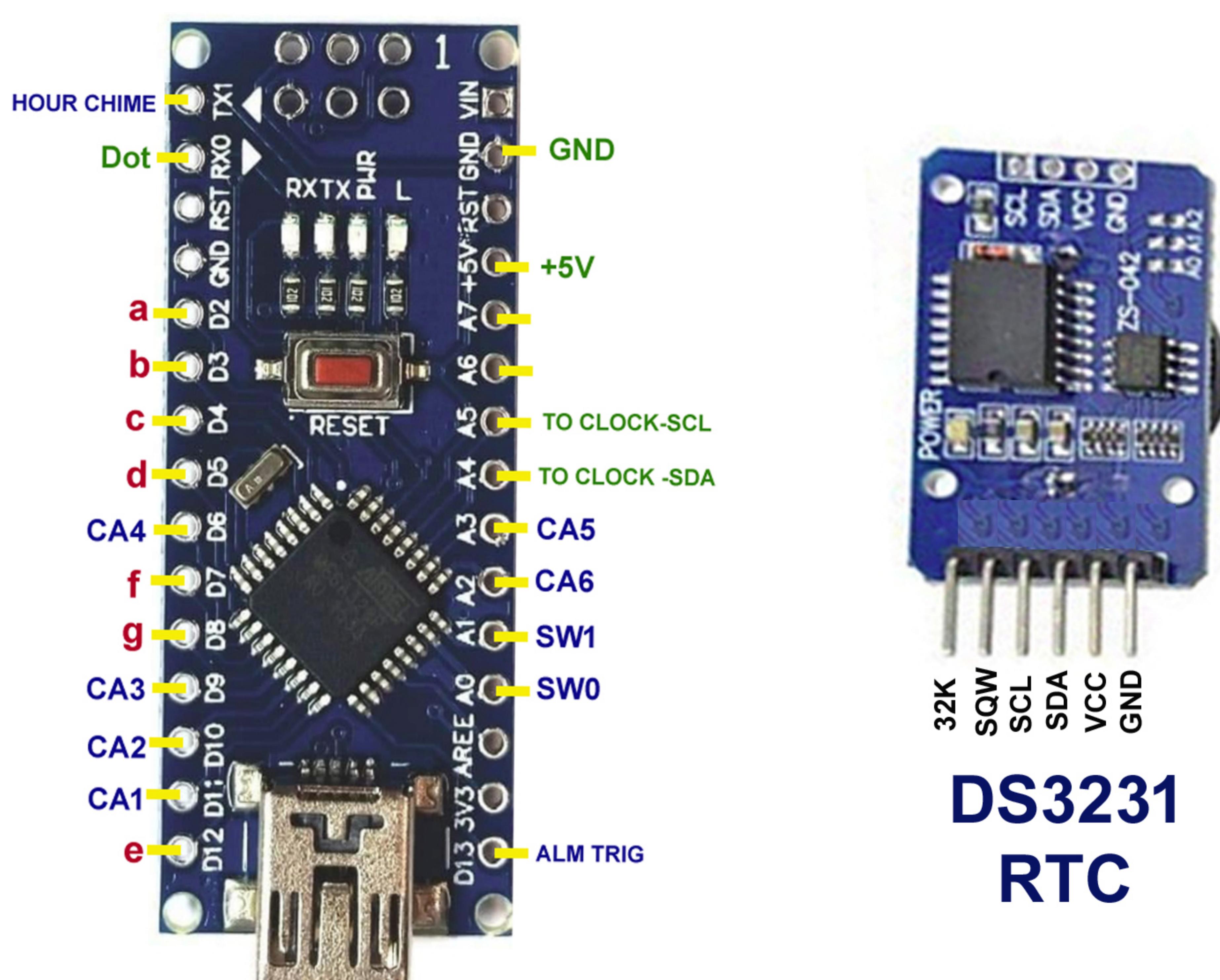


**DISPLAY**



**ARUNINO NANO**

## HOUR CHIME MUSIC GENERATOR USING UM66

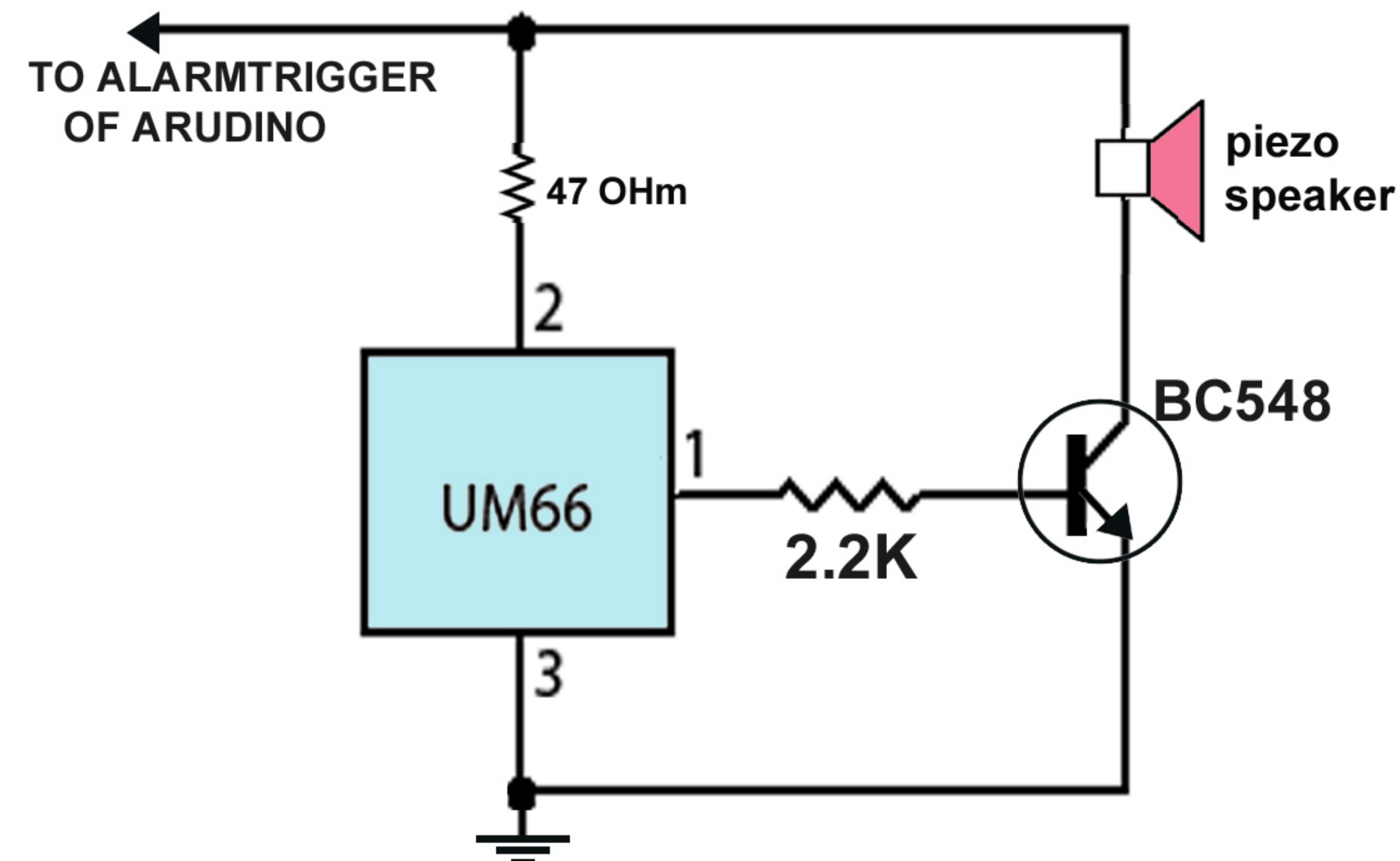

## ALARM BEEPER WITH 555 IC

